



# Synthesis for Security

2023.12.26



R12943102 **王濊紳**

R12943103 **張芯慈**

# Outline

- IC camouflaging
- Logic Obfuscation
- Statistics

# Layout-level Approach: IC Camouflaging

  

- Replace some gates with camouflaged gates
- Attacker cannot verify functionality from layout directly


# IC Camouflaging – Threat Model

- The attacker can **delayer** the IC by optical microscope and image processing tool
- The attacker can **differentiate regular/camouflaged standard cells**
- The attacker knows the **list of possible functions** a camouflaged cell can implement. E.g. {XOR, NAND, NOR}

# IC Camouflaging – Objective


- Given the original circuit, choose a set of standard cells for camouflaging
  - Goal: effectively increase the complexity of resolving the functionality of each camouflaged gate
  - **Design overhead** should be considered
- ⇒ Given the original circuit, choose **a certain percentage of** standard cells for camouflaging

# Different Status of Camouflaged Gates

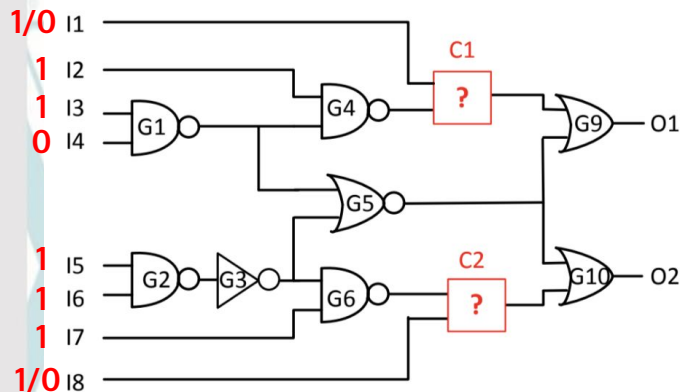


Isolated

Easy to Attack

 

Partially resolvable

 

Non-resolvable

Hard to Attack



# Output Corruptibility

Output corruptibility

$$= \sum_{\# \text{ I/P patterns}} (\# \text{ O/Ps with ambiguity activated and propagated})$$

- Higher output corruptibility  
⇒ More impact on incorrect function selection

# IC Camouflaging – Defender Strategy


- Assume desired number of camouflaged gates =  $N$
- First, camouflage the gate with **highest output corruptibility**
- For  $i = 2$  to  $N$ ,
  - Identify all **non-resolvable** uncamouflaged gates based on the camouflaged gates as candidates
  - Among all candidates, select the one with **highest output corruptibility**



# Gate-level Approach: Logic Obfuscation

- Introduction: Key-Gates insertion
- Key-Gates Structures
- Defend Algorithm

# Gate-level Approach: Logic Obfuscation

 

- Insert XOR/XNOR gates
- With incorrect keys, circuit behavior would differ from the original one

# Key-Gates Structures

- Runs of key-gates
- Isolated key-gates
- Mutable key-gates
  - Dominating key-gates
  - Concurrent key-gates
  - Sequential key-gates
- Non-Mutable key-gates


Unsafe

Safe



# Runs of key-gates


- Meaningless PPA overhead
- **Single key-bit** from attacker perspective

 

**Figure 4:** (a) A run of two key-gates K1 and K2. (b) K3 replaces K1 and K2.

 
# Isolated key-gates

- No path to all other key-gates
- Can be solved as one bit key


 
# Isolated key-gates


- No path to all the other key-gates
- Can be solved as one bit key






# Mutable key-gates

- $A=1$  or  $B=0$  mute Key1 or Key2

 

# Non-mutable key-gates


- Attacker must apply brute force

 

# Defend Algorithm

- Assumption of attacker
  - Know the location of key gate
  - Able to brute-force all the PI-PO relations
  - NOT able to rewire or observe internal logic
- Strategy on key-gates
  - No run of key-gates
  - Isolated key-gates (metric = 0)
  - Mutable key-gates (metric = 1)
    - Dominating, Concurrent, Sequential
  - Non-mutable key-gates (metric = 2)

# Defend Algorithm

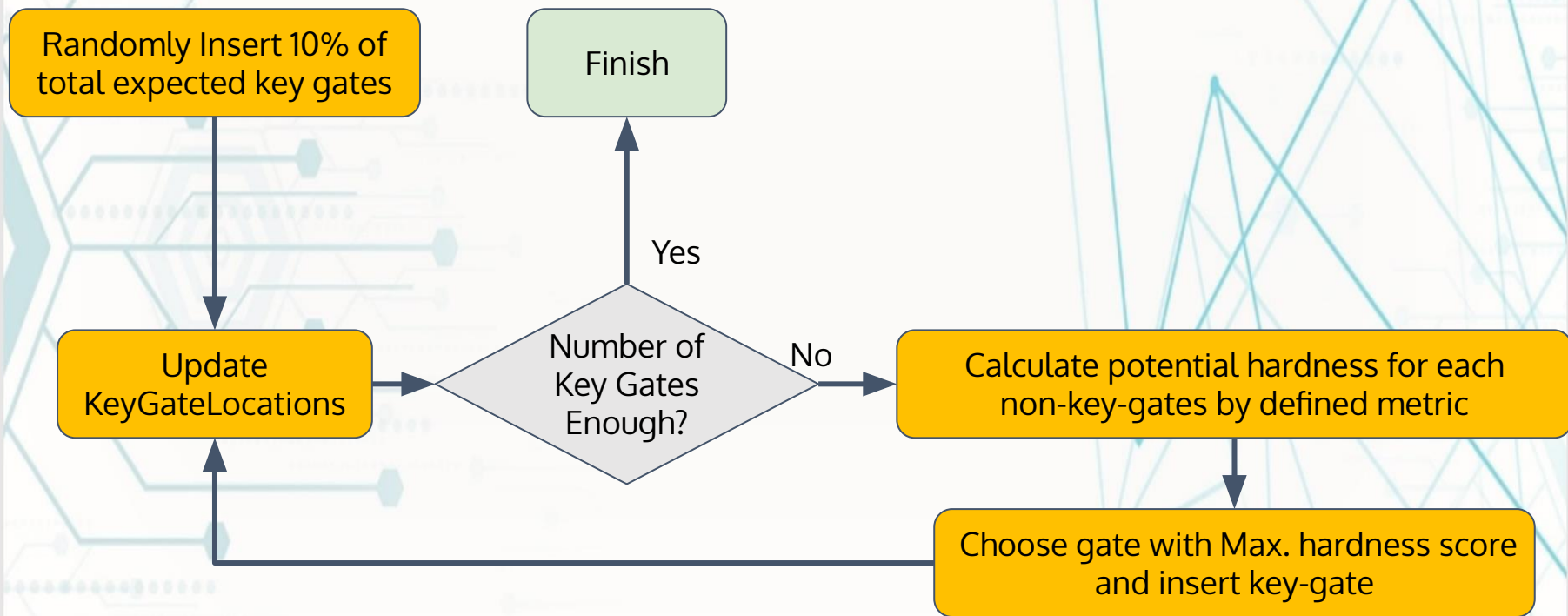

# Implementation Setup

- Defend Algorithm Metric used: isolated=0, non-isolated=1
- Area: abc gate count
- Delay: abc levels

# Example: before obfuscation

```
module c17(N1, N2, N3, N6, N7, N22, N23);  
    input N1, N2, N3, N6, N  
    output N22, N23;  
    wire N3; N2, N3, N6, N7, N10, N16, N11, N19, N22, N23;  
    assign N10 = ~( N1 & N3 );  
    assign N16 = ~( N2 & N11 );  
    assign N11 = ~( N3 & N6 );  
    assign N19 = ~( N11 & N7 );  
    assign N22 = ~( N10 & N16 );  
    assign N23 = ~( N16 & N19 );  
endmodule
```



# Example: after obfuscation

```
module c17(N1, N2, N3, N6, N7, key_0, key_1, key_2, N22_key, N23_key);
  input N1, N2, N3, N6, N7;
  input key_0, key_1, key_2;
  output N22_key, N23_key;
  wire N1, N2, N3, N6, N7, N10, N16, N11, N19, N22, N23;
  wire N23_key, N22_key, N1_key;
  wire key_0, key_1, key_2;
  assign N10 = ~( N1_key & N3 );
  assign N16 = ~( N2 & N11 );
  assign N11 = ~( N3 & N6 );
  assign N19 = ~( N11 & N7 );
  assign N22 = ~( N10 & N16 );
  assign N23 = ~( N16 & N19 );
  assign N23_key = ~( N23 ^ key_0 );
  assign N22_key = ~( N22 ^ key_1 );
  assign N1_key = ~( N1 ^ key_2 );
endmodule
```

# Implementation Statistics

Circuit	Original		Obfuscated		Overhead	
	Area	Delay	Area	Delay	Area	Delay
c880	325	25	397	31	18.14%	19.35%
c1355	494	25	584	33	15.41%	24.24%
c3540	1034	41	1097	50	5.74%	18.00%
c5315	1774	37	2146	38	17.33%	2.63%
c6288	2337	120	2445	122	4.42%	1.64%

# Reference

- [1] J. Rajendran, Y. Pino, O. Sinanoglu and R. Karri, "Security analysis of logic obfuscation," DAC Design Automation Conference 2012, San Francisco, CA, USA, 2012, pp. 83-89
- [2] Jeyavijayan Rajendran, Michael Sam, Ozgur Sinanoglu, and Ramesh Karri. 2013. Security analysis of integrated circuit camouflaging. In Proceedings of the 2013 ACM SIGSAC conference on Computer & communications security (CCS '13). Association for Computing Machinery, New York, NY, USA, 709–720.
- [3] Jarrod A. Roy, Farinaz Koushanfar, and Igor L. Markov. 2008. EPIC: ending piracy of integrated circuits. In Proceedings of the conference on Design, automation and test in Europe (DATE '08). Association for Computing Machinery, New York, NY, USA, 1069–1074.

Thanks for your attention !




# Why Synthesis for Security

- Prevent IP piracy
- Add ambiguity to increase the difficulty for reverse engineering
 
# Dominating key-gates (mutable)


- Key2 dominates Key1
- **Mute** Key1 to solve Key2




 
# Concurrent key-gates (mutable)

- $A=1$  or  $B=0$  mute Key1 or Key2 ( $\Leftrightarrow$ )



# Sequential key-gates (mutable)

- A=1, Mute key1 to solve key2 ( $\Rightarrow$ )
- Key2 not mutable

